
 


This lecture discusses how to actually measure syndromes for CSS codes in a fault-tolerant manner.

 First thing to review is some notation for quantum circuits which will be more useful than writing out sequences of unitaries.



The most common gates we'll be using are:



let's now build the circuits needed for syndrome extraction in a CSS code.


Key issues: ① DO NOT measure $Z_1 Z_2 Z_3 Z_4$ by measuring Z_1 , then $Z_2, \dots$

② most experiments can only do 2-qubit gates

Resolve: add ancilla qubits to help w/ syndrome extraction
data qubits: physical qubits of QEC code

Recall:
$$\text{CNOT}_{1 \rightarrow 2} \begin{pmatrix} x_1 \\ x_2 \\ z_1 \\ z_2 \end{pmatrix} \overset{= \text{CNOT}_{1 \rightarrow 2}^\dagger}{\text{CNOT}_{1 \rightarrow 2}} = \begin{pmatrix} x_1 x_2 \\ x_2 \\ z_1 \\ z_1 z_2 \end{pmatrix}$$

 Alg (Z-check syndrome extraction): to measure $z_1 z_2 z_3 z_4$:



Important that we start ancilla in a known state. To see why it works, notice that **at initial time, stabilizer $Z_a = +1$**

$$\text{CNOT}_{1 \rightarrow a} Z_a \text{CNOT}_{1 \rightarrow a} = Z_1 Z_a \Rightarrow \text{final stabilizer } \underbrace{Z_1 Z_2 Z_3 Z_4 Z_a}_{= +1}$$

Measure $Z_a \Rightarrow$ outcome tells us $Z_1 Z_2 Z_3 Z_4$ or: $Z_a = Z_1 Z_2 Z_3 Z_4$

Example: Start in $|\psi_0\rangle = \frac{1}{2} [\underbrace{|0000\rangle}_{+} + \underbrace{|1111\rangle}_{+} + \underbrace{|0001\rangle}_{-} + \underbrace{|1110\rangle}_{-}] \otimes |0\rangle$


What's final outcome?

$$|\psi_{\text{final}}\rangle = \begin{cases} \frac{1}{\sqrt{2}} [|0000\rangle + |1111\rangle] \otimes |0\rangle & \text{w/ prob. } 1/2 \\ \frac{1}{\sqrt{2}} [|0001\rangle + |1110\rangle] \otimes |1\rangle & \text{w/ prob. } 1/2 \end{cases}$$

$\Rightarrow$ **error digitization** as we should expect from theory of QEC

Straightforward to generalize this algorithm to measure a Z-check of any size.

 Alg (X-check syndrome extraction): to measure $X_1 X_2 X_3 X_4$,



Initial time: stabilizer $X_{a'} = +1$


$\text{CNOT}_{a' \rightarrow 1} X_{a'} \text{CNOT}_{a' \rightarrow 1} = X_1 X_{a'} \Rightarrow$ final stabilizer $X_1 X_2 X_3 X_4 X_{a'}$

Measure $X_{a'} = X_1 X_2 X_3 X_4$ to collapse code into syndrome eigenspace!

Key thing is that these circuits only used 2-qubit gates... if expt has higher-order gates then those may also be useful.

Now need to discuss fault-tolerance of this protocol...

 Focus on Z-syndrome extraction since analogous story for X...



Note: errors depicted here like unitaries but same story applies for more general channels...

error E_1 on physical qubit after CNOT:

$E_1 = Z \Rightarrow$ "no effect" here (it'll be picked up during X-syndrome extraction...)

$E_1 = X \Rightarrow$ undetected error!

Nice way to see this is by pushing through E_1 to one end of the syndrome extraction circuit:

$$E_1 \text{CNOT}_{1 \rightarrow a} = \text{CNOT}_{1 \rightarrow a} \cdot (\text{CNOT}_{1 \rightarrow a} E_1 \text{CNOT}_{1 \rightarrow a}) \begin{matrix} \xrightarrow{\text{red}} \\ Z_1 \rightarrow Z_1 \\ X_1 \rightarrow X_1 X_a \end{matrix}$$

$\Rightarrow X_1$ error becomes $X_1 X_a \Rightarrow$ syndrome outcome opposite:
 $X_1 X_2 X_3 X_4 X_a = -1$

So this error can enhance probability of a faulty syndrome outcome.

error E_2 on ancilla during extraction:

$E_2 = X_a \Rightarrow$ syndrome outcome wrong

$E_2 = Z_a \Rightarrow$ hook error

$$\begin{aligned} Z_a \text{CNOT}_{12 \rightarrow a} &= \text{CNOT}_{12 \rightarrow a} (\text{CNOT}_{12 \rightarrow a} Z_a \text{CNOT}_{12 \rightarrow a}) \\ &= \text{CNOT}_{12 \rightarrow a} \underbrace{Z_1 Z_2}_{\text{hook error}} \underbrace{Z_a}_{\substack{\text{harmless} \\ \text{stabilizer}}} \end{aligned}$$

Note: hook error $Z_1 Z_2$ stabilizer-equiv. to $Z_3 Z_4$. check weight
 worry: correlated Z-errors (hook) of weight $\leq \lfloor \frac{1}{2} \Delta_C \rfloor$
 arise during noisy syndrome extraction

$\Rightarrow$ "engineering" problem: circuit-level fault-tolerance


$\Rightarrow$ threshold for correlated errors generated thru these circuits

One generally resorts to large-scale numerical studies using G-K algorithm to efficiently simulate circuit-level noise.


circuit-level noise $\Rightarrow$ threshold at $p \sim 0.01$ (not 0.03)
 for standard (MWPM) decoder

Indeed let's now see how circuit-level noise complicates syndrome extraction for (rotated) surface code...

 Issue #1: hook errors can reduce the effective distance.



 Recall the setup of the rotated surface code



Measuring Z-check $\Rightarrow$ Z-hook error possible b/w first 2 measured qubits (equiv. to last 2)


Syndrome extraction $1 \rightarrow 2 \rightarrow 3 \rightarrow 4$ causes hook error aligned w/ logical
 $\Rightarrow d_{\text{eff}} \approx d/2$

instead choose $1 \rightarrow 4 \rightarrow 3 \rightarrow 2$ so Z-hook error doesn't align w/ any lowest-weight Z-logical

Similar strategy arises for X-syndrome extraction...


Issue #2: CNOT scheduling.

 Ideally, weight-4 checks measured in 4 rounds.
 $\Rightarrow$ (most) qubits in a CNOT in each layer of circuit:




Consider a patch of surface code w/ checks $X_1, X_2, \dots$ $Z_1, Z_2, \dots$ checks to measure.

bad circuit layout:

 

good circuit layout:

 

We can see the issue by evolving final measurement outcome backward through circuit...

$$U_{\text{bad}}^\dagger Z_{a_2} U_{\text{bad}} = Z_1 Z_2 \underbrace{Z_{a_x}}_{\text{unwanted!!}} Z_{a_2} \quad \text{not a stabilizer of initial state}$$

$$U_{\text{good}}^\dagger Z_{a_2} U_{\text{good}} = Z_1 Z_2 \underbrace{Z_{a_2}}_{=+1 \text{ at start, meaning we measure } Z_1 Z_2 \text{ at the end}}$$

in principle, fault-tolerance for generic qLDPC.

Why? - finite rounds of syndrome extraction for all checks
 $\Rightarrow$ limits idling errors
 - finite-size hook errors w/ 2-qubit gates...

Since one error might duplicate in hook, estimate

$$P[\text{logical fail}] \sim n p_c^{d/(\Delta_c/2)} \quad \text{in worst case}$$

So LDPC still important to ensure

$$d \gg \log n \Rightarrow P[\text{logical fail}] \rightarrow 0$$